

Practical: 5**Aim: Design 4-bit Combinational Circuit Shifter.****Theory:**

Shift micro-operations are used for serial transfer of data. They are also used in conjunction with arithmetic, logic and other data-processing operations. The contents of a register can be shifted to the left or the right. At the same time that the bits are shifted, the first flip-flop receives its binary information from the serial input. During a shift-left operation the serial input transfers a bit into the rightmost position. During a shift-right operation the serial input transfers a bit into the leftmost position.

Select	Output			
S	H ₀	H ₁	H ₂	H ₃
0	I _R	A ₀	A ₁	A ₂
1	A ₁	A ₂	A ₃	I _L

Table: Function table

The content of a register that has to be shifted is first placed onto a common bus whose output is connected to the combinational shifter, and the shifted number is then loaded back into the register. A combinational circuit shifter can be constructed with multiplexers as shown in Fig A. The 4-bit shifter has four data inputs, A₀ through A₃, and four data outputs, H₀ through H₃. There are two serial inputs, one for shift left (I_L) and the other for shift right (I_R). When the selection input S = 0, the data are shifted right. When S = 1, the input data are shifted left. The function table shows input goes to each output after the shift. A shifter with n data input outputs requires n multiplexers.

Procedure:

1. Create the circuit as per function table.
2. Verify the function table for each operation.

Circuit Diagram: