

Practical: 6**Aim: Implement Circuit for Logic Micro operations.****Theory:**

Logic micro operations refer to the logic operations on bits of a pair of register or single register. Following table shows the some logic micro operations.

Function	Micro operations
Clear	$C_1 : A \leftarrow 0$
AND	$C_2 : A \leftarrow A \cdot B$
OR	$C_3 : A \leftarrow A + B$
EX-OR	$C_4 : A \leftarrow A \oplus B$
Complement	$C_5 : A \leftarrow \bar{A}$

Circuit Diagram: